
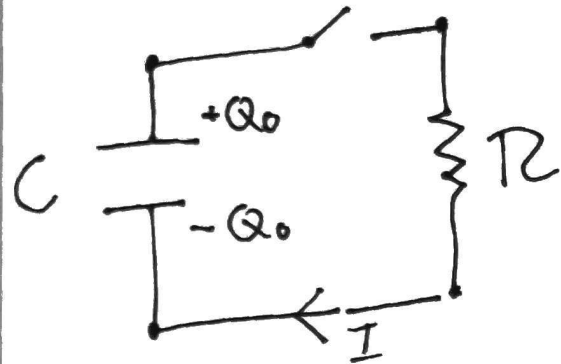


RC Circuits

↳ Non-equilibrium, transient behavior

• Discharging

↳ C initially charged
 $Q(t=0) = Q_0$

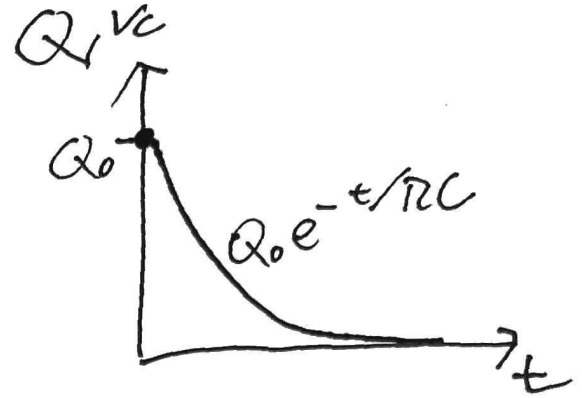

Close the switch

⇒ Allows current to flow until steady-state is reached.

• Charge Cons.

$$\boxed{I = -\frac{dQ}{dt}}$$

$\left. \begin{aligned} &V_C = 0 \\ &\Rightarrow Q = 0 \\ &(t = \infty) \end{aligned} \right\} \frac{dQ}{dt} = 0$

• Loop rule: $V_C = V_R$


$$\hookrightarrow \frac{Q(t)}{C} = R \cdot I(t) = -R \frac{dQ}{dt}$$

$$\Rightarrow \frac{dQ}{dt} = -\frac{Q(t)}{RC} \Rightarrow$$

$$\boxed{Q(t) = Q_0 e^{-t/RC}}$$

$$\begin{aligned} \frac{d}{dt}[Q(t)] &= Q_0 \left(\frac{-1}{RC} e^{-t/RC} \right) \\ &= -\frac{Q(t)}{RC} \checkmark \end{aligned}$$


• Charging

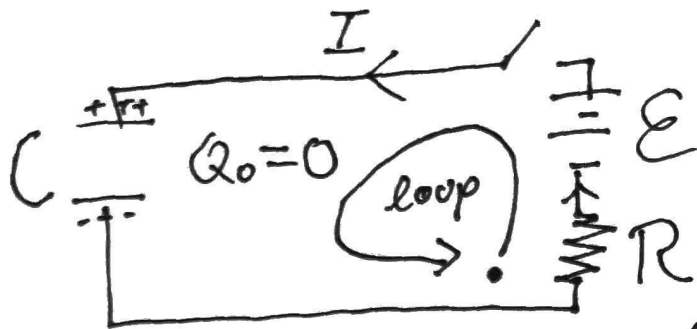

C initially uncharged

$$Q(t=0) = 0$$

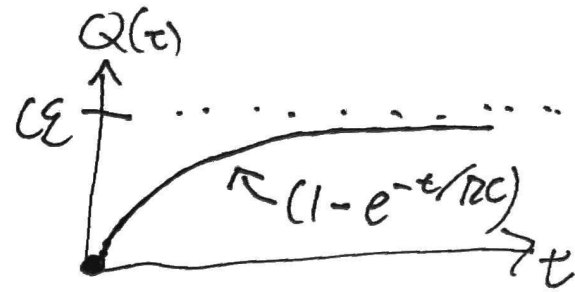Close the switch
 \Rightarrow Current to flow



Charge cons.

Steady state: $t = \infty$, $Q = Q_{\infty}$,

$$I = + \frac{dQ}{dt}$$

$$V_R = IR = 0$$

$$\Rightarrow V_C(t = \infty) = \mathcal{E} \Rightarrow Q_{\infty} = C \cdot V_C = CE$$

- Loop rule ($-V_C - V_R + \mathcal{E} = 0$)

$$-I(t)R + \mathcal{E} - \frac{Q(t)}{C} = 0$$

$$\mathcal{E} = \frac{Q(t)}{C} + \frac{dQ}{dt} R$$


$$\hookrightarrow \boxed{\frac{dQ}{dt} + \frac{Q(t)}{RC} = \frac{\mathcal{E}}{R}}$$

$$\boxed{Q(t) = (1 - e^{-t/RC}) \underbrace{CE}_{Q_{\infty}}}$$

$$\left(\frac{d}{dt} [\quad] = + \frac{CE}{RC} e^{-t/RC} \right)$$

$$\frac{Q(t)}{RC} + \frac{dQ}{dt} = \frac{CE}{RC} = \frac{\mathcal{E}}{R} \quad \checkmark$$

⌊ (Giancoli 26.49)

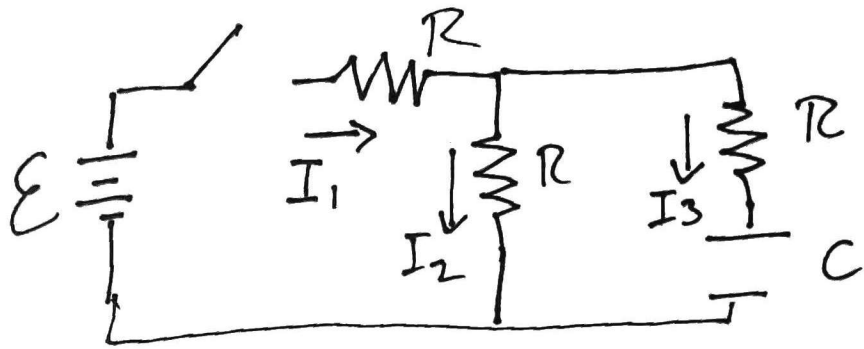

$t=0$, C is uncharged
 \Rightarrow Close the switch

\hookrightarrow Look at $t=0$, $t=\infty$ behavior.


Often we can consider a simpler, effective circuit.

(a) At $t=0$, what are the currents?

$$\hookrightarrow Q(0)=0$$

$$\Rightarrow V_C(0) = Q/C = 0$$

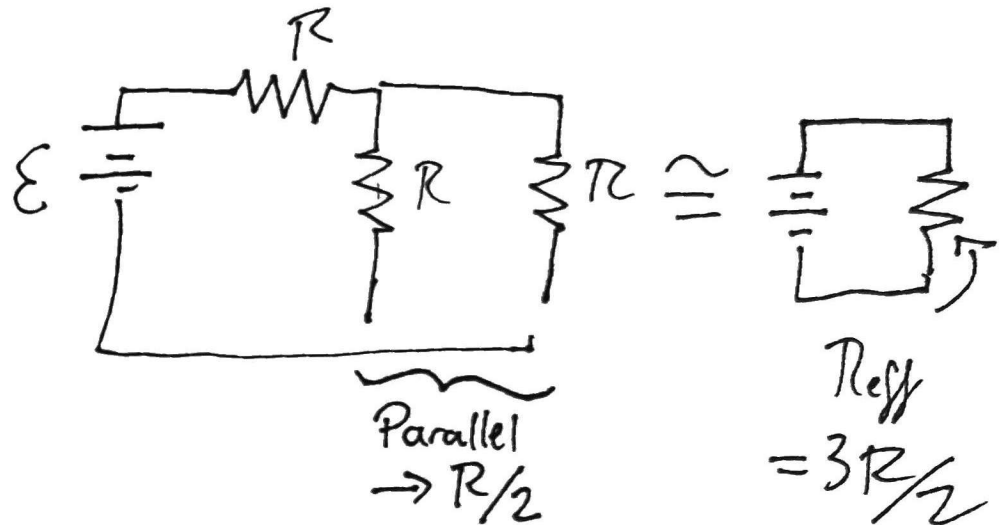$V_{top} = V_{bot} \Rightarrow$ I can replace C with wire.




$$\Rightarrow I_1 = \frac{\epsilon}{R_{eff}} = \frac{2\epsilon}{3R}, \quad I_2 = I_3 \text{ (sym.)}$$

$$= \frac{\epsilon}{3R} \text{ (Junc. rule)}$$

(b) Currents at $t = \infty$?


Q_c has reached a constant Q_{∞}

$$\Rightarrow \frac{dQ_c}{dt} = 0$$

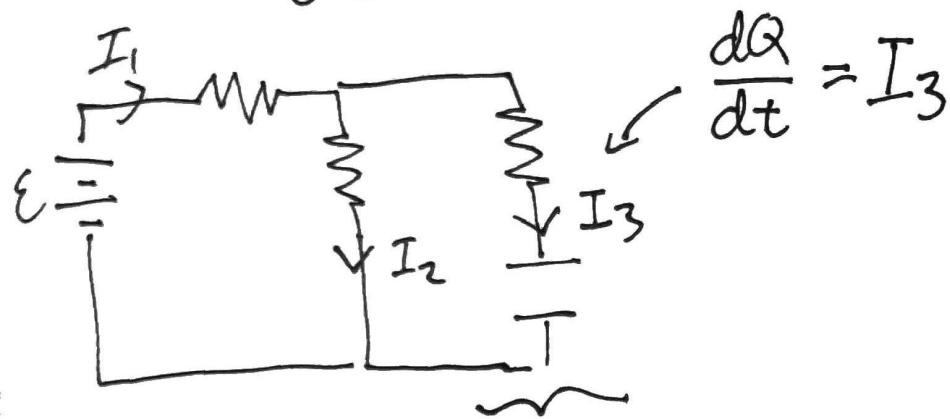


$$\boxed{I_3 = \frac{dQ}{dt} = 0} \quad \text{at } t = \infty$$

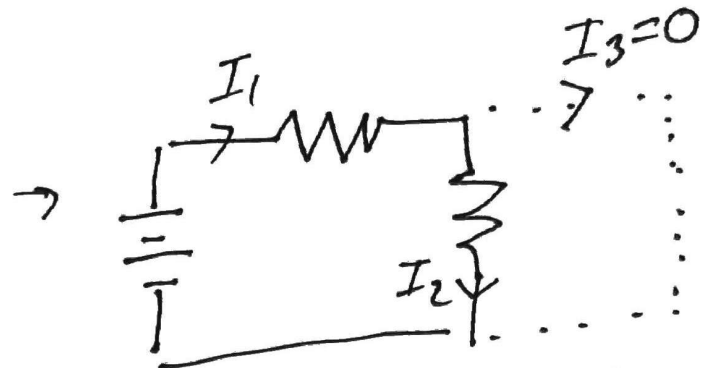\Rightarrow Remove the right branch from circuit.



$$\Rightarrow \boxed{I_1 = I_2 = \frac{\mathcal{E}}{R_{\text{eff}}} = \frac{\mathcal{E}}{2R}}$$

(c) At $t = \infty$, what is V_c , Q ?

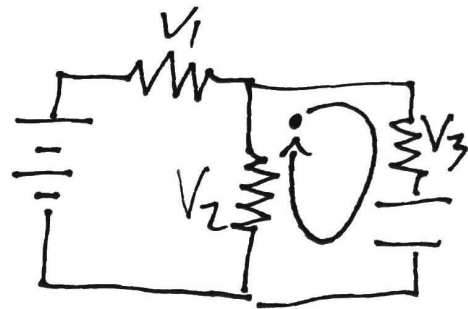

Loop rule:

$$V_2 = V_3 + V_c$$

$$I_2 R = I_3 R + V_c$$

$$\frac{\mathcal{E}}{2R} \cdot R \quad 0$$

$$\boxed{Q_{\infty} = CV_c = C\mathcal{E}/2}$$

$$\Rightarrow \boxed{V_c = \mathcal{E}/2}$$


(b) $t = \infty$?

Q_c has reached a constant val.

$$\hookrightarrow \frac{dQ_c}{dt} = 0$$

||


$$I_3$$

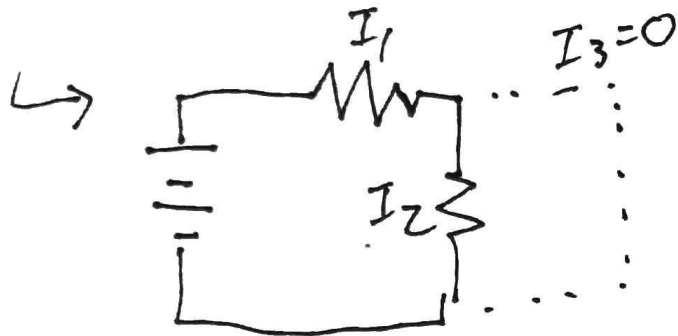


$$I_1 = I_2 = \frac{\mathcal{E}}{2R}$$

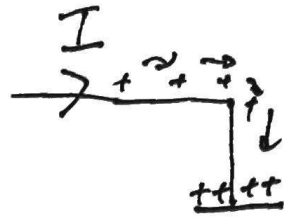(c) $t = \infty$, what is V_c ?


$$\hookrightarrow R \parallel C \quad V = I_2 R = \mathcal{E}/2$$



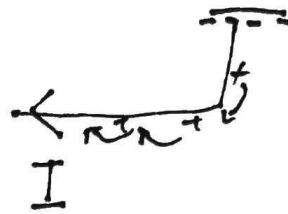\leftarrow + charge gets stuck / builds up



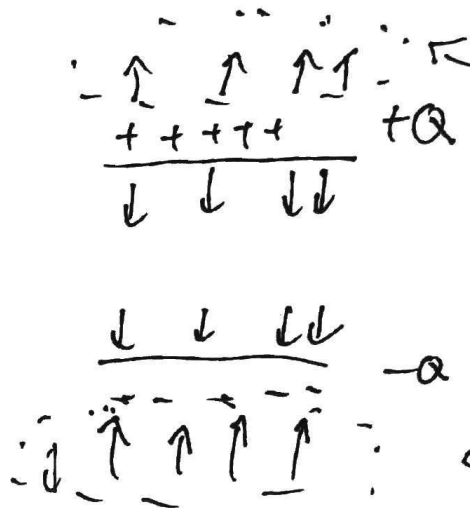\leftarrow + charge pulled off of negative plate.




Unless Q on top and bot plates are equal,

\Rightarrow need E -field.

\hookrightarrow Will push or pull charge until equalized.

2] (Grancollis 26.50)

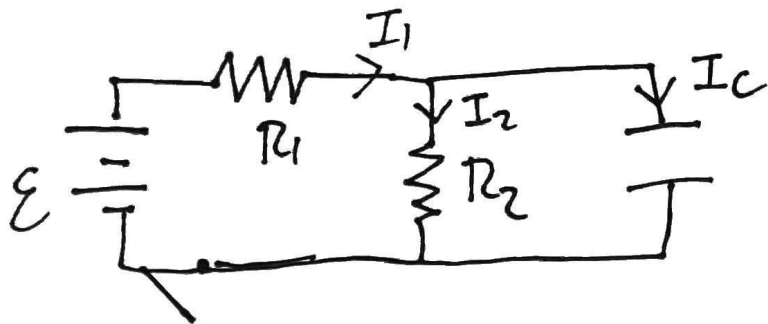


Initially, C uncharged.

↳ Close switch at $t=0$.

Charging process

↳ I expect something like
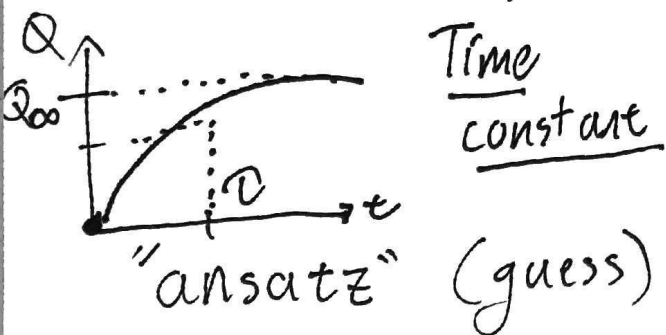
$$Q(t) = (1 - e^{-t/\tau}) \cdot Q_{\infty}$$



(a) Determine τ (time const.)


(b) Find Q_{∞}

↳ $t = \infty$, $Q = Q_{\infty}$ const

$$\frac{dQ}{dt} = 0 \quad (t \rightarrow \infty)$$


↳ $I_C = 0$

Simpler
eff. circuit:

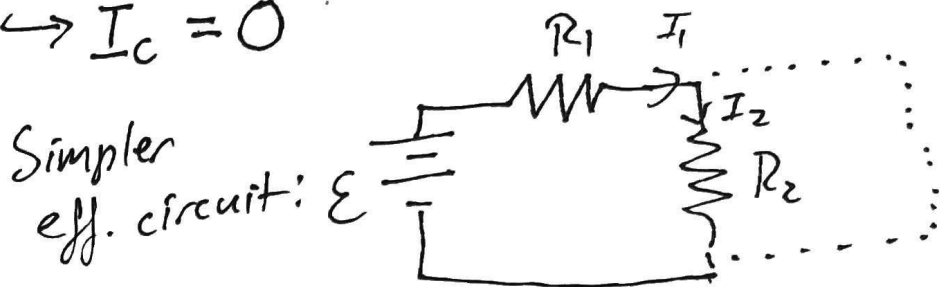

$$I_1 = I_2 = \frac{\varepsilon}{R_{\text{eff}}} = \frac{\varepsilon}{R_1 + R_2}$$

Loop
rule:

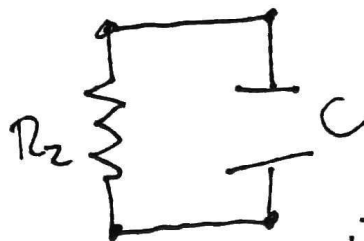


$$V_2 = V_C$$

$$I_2 R_2 = Q_{\infty} / C$$

$$Q_{\infty} = \varepsilon \cdot \frac{R_2}{R_1 + R_2} \cdot C$$

(✓ works
work) →

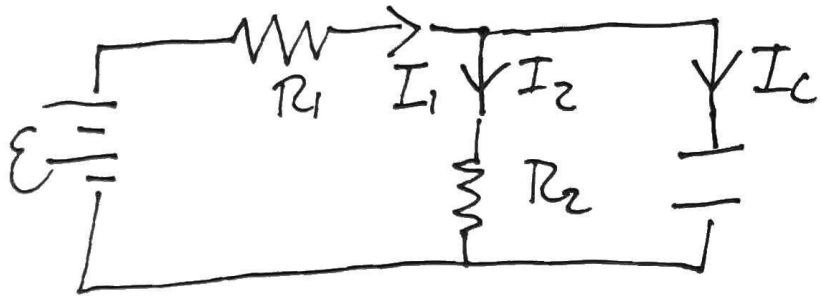(a)(i) Use Kirchoff laws
(analyze circuit from scratch)



Junction rule:


$$I_1 = I_2 + I_C$$

Loop rule:

Left loop -

$$0 = +\varepsilon - I_1 R_1 - I_2 R_2$$


$$\varepsilon = I_1 R_1 + I_2 R_2$$

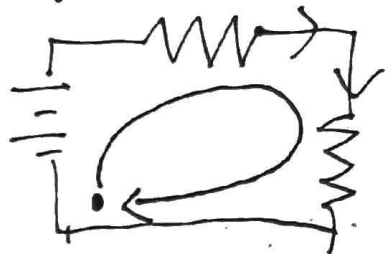

Right loop

$$\Rightarrow V_C = I_2 R_2$$

$$\frac{Q}{C} = I_2 R_2$$

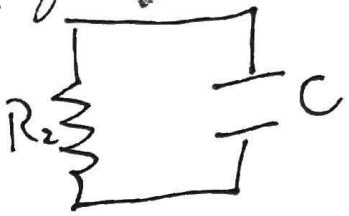

(ii) * RC circuit strategy *

Rewrite all the I
in terms of Q, $\frac{dQ}{dt}$.

$$I_C = \frac{dQ}{dt}$$

$$I_2 = \frac{Q}{R_2 C}$$

$$I_1 = \frac{Q}{R_2 C} + \frac{dQ}{dt}$$

(iii) Use leftover equation
to get Q, $\frac{dQ}{dt}$ relationship
(ODE).

$$\varepsilon = R_1 \left[\frac{Q}{R_2 C} + \frac{dQ}{dt} \right] + \frac{Q}{C}$$

ε, R_1, R_2, C are constants

(iv) Try to solve:

$$\mathcal{E} = R_1 \left[\frac{Q}{R_2 C} + \frac{dQ}{dt} \right] + \frac{Q}{C}$$

$$\frac{\mathcal{E}}{R_1} = \frac{Q}{R_2 C} + \frac{Q}{R_1 C} + \frac{dQ}{dt}$$

$$= \frac{Q}{C} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{dQ}{dt}$$

$$= R_{12}^{-1} \equiv \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

(Parallel formula for R)

$$\boxed{\frac{\mathcal{E}}{R_1} = \frac{Q}{R_{12} C} + \frac{dQ}{dt}}$$

↳ Solve

↳ or, try the ansatz:

$$Q(t) = Q_{\infty} (1 - e^{-t/\tau})$$

(earlier \hookleftarrow)

$$Q_{\infty} = C \mathcal{E} \cdot \frac{R_2}{R_1 + R_2}$$

$$\frac{\mathcal{E}}{R_1} = \frac{Q_{\infty}}{R_{12} C} (1 - e^{-t/\tau}) + \frac{Q_{\infty}}{\tau} e^{-t/\tau}$$

Rewrite:

(Divide by Q_{∞} ,
move const. over)

$$\boxed{\left(\frac{\mathcal{E}}{R_1 Q_{\infty}} - \frac{1}{R_{12} C} \right) = \left(\frac{1}{\tau} - \frac{1}{R_{12} C} \right) e^{-t/\tau}}$$

$$\begin{aligned}
 \text{LHS: } \frac{\mathcal{E}}{R_1} - \frac{1}{R_{12}C} &= \frac{\mathcal{E}}{R_1} \left(\frac{1}{C\mathcal{E}} \frac{R_1 + R_2}{R_2} \right) - \frac{1}{R_{12}C} \\
 &= \frac{R_1 + R_2}{C R_1 R_2} - \frac{1}{R_{12}C} \\
 &= \frac{1}{R_{12}C} - \frac{1}{R_{12}C} = 0
 \end{aligned}$$

$$\Rightarrow \text{RHS} = 0$$

$$\left(\frac{1}{\tau} - \frac{1}{R_{12}C} \right) e^{-t/\tau}$$

$$\Rightarrow \boxed{\tau = R_{12}C}$$

$$R_{12} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$